

## 5.4 Cells in series and parallel

## Diodes in circuits

AS27

### 5.4 Cells in Series and Parallel

#### (i) Cells in series

- When cells are connected in series, the total emf is the sum of the emfs of each cell.
- The current through each cell is the same.

$$\text{cell current} = \frac{\text{cell emf}}{\text{total circuit resistance}}$$

- The 'lost volts'  $\varepsilon - V = I(\text{sum of internal resistances})$


#### (ii) Cells in parallel

- When identical cells are connected in parallel, the total emf is equal to the emf of each cell.
- The total current supplied is the sum of the currents through each. If there are  $n$  cells and the total current is  $I$ , the current through each cell is  $I/n$ .
- The total 'lost volts' is given by:


$$\varepsilon - V = \frac{Ir}{n}$$
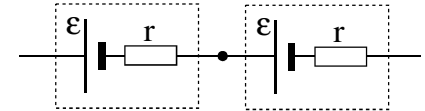
#### Diodes in circuits


- In forward bias, a p.d. of 0.6 volts exists across a semiconductor diode if it is passing a current.
- In reverse bias, the diode has a near infinite resistance.




Cells in series

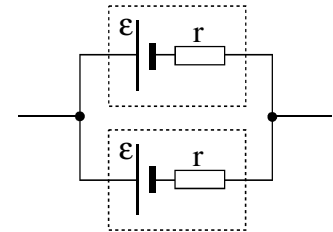

Cells in parallel

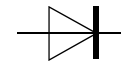

current in  
forward bias

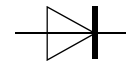

current in  
reverse bias

## 5.5 The potential divider

AS27

### 5.5 The Potential Divider

The potential divider is a combination of two or more resistors in series. A power supply is connected across all the resistors and various p.d.s can be tapped of the combination. The resistors can be fixed or variable, giving a device which can provide a fixed output, a variable pd. output or an output p.d. that changes with some physical condition such as light level or temperature.

For the stepped output in figure 1,

$$V_{out} = \left( \frac{R_3}{R_1 + R_2 + R_3} \right) V_{in}$$

If one of the resistors in a potential divider combination is made variable, a continuously variable output can be achieved, as shown in figure 2.

$$V_{out} = \left( \frac{R_1}{R_1 + R_2} \right) V_{in}$$

Sensor circuits are often controlled by a potential divider in which the sensor, (a thermistor or light-dependent resistor, for example), is one of the resistors. The other resistor is variable to adjust the temperature or light level at which the sensor circuit switches on.

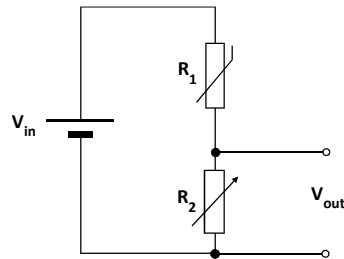


Fig 3

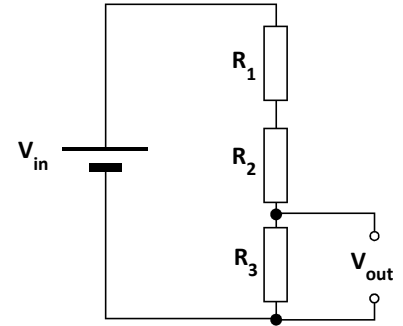


Fig 1

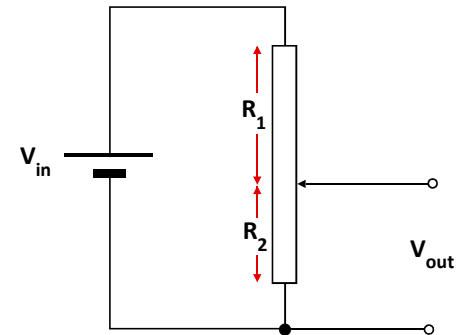


Fig 2